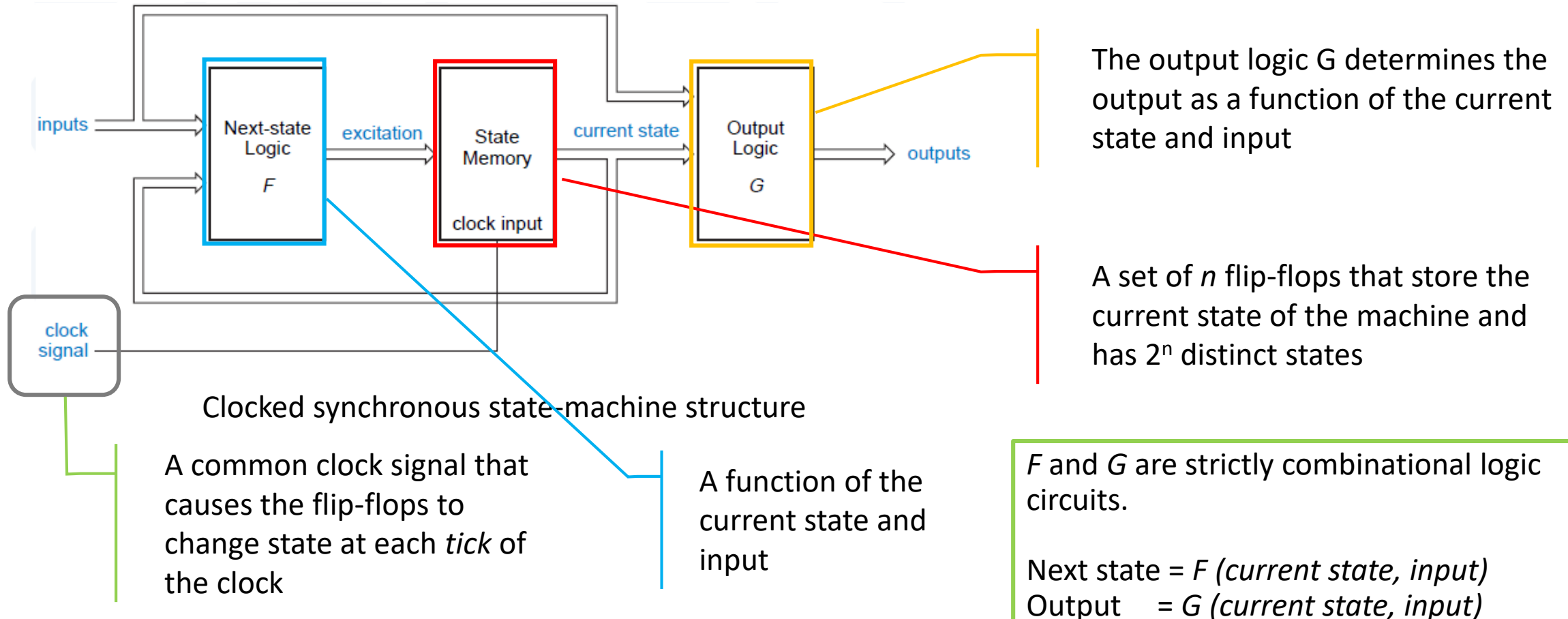


Pakorn Watanachaturaporn
pakorn.wa@KMITL.ac.th


01076244 Advanced Digital System Design

Bachelor Program in Computer Engineering (B.Eng.)
Faculty of Engineering
King Mongkut's Institute of Technology Ladkrabang


State-Machine Structure



Output Logic

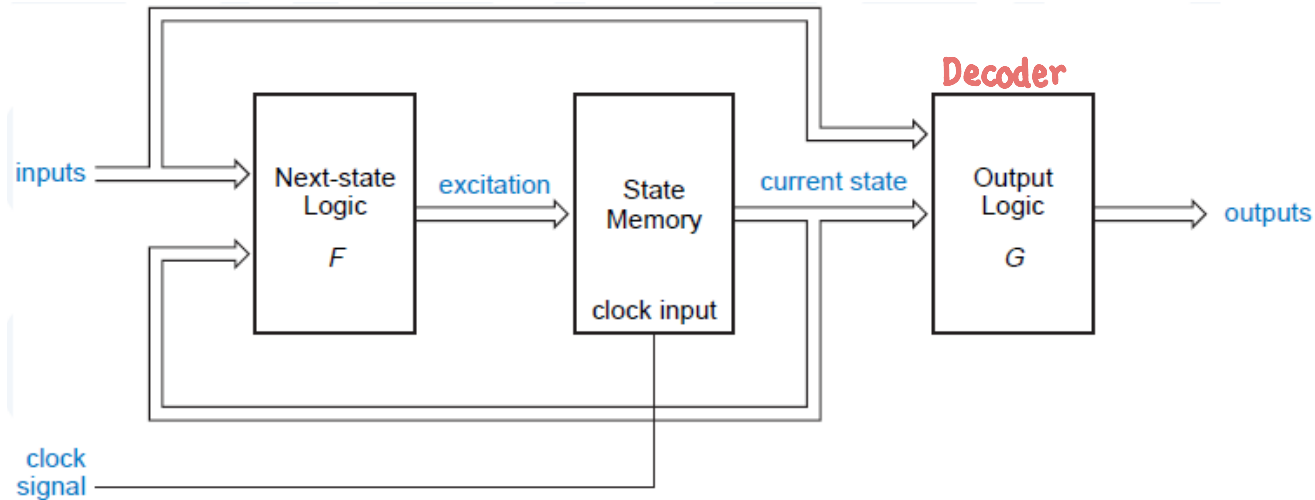

 Mealy machine : output depends on both **state** and **input**



Moore machine : the output depends on **state** alone


Characteristic Equations

- A Characteristic equation ^{ทำให้ logic เป็น สมการ ทวคณิตศาสตร์ ที่ ระบุว่ามันทำงานเป็นไร} is a formally description of a fⁿ behavior
- The * suffix means the “next value”
- Note: the characteristic equation does not describe detailed timing behavior of the device (latching vs. edge-triggered, etc.), only the fⁿ response to the control input

Device Type	Characteristic Equation
S-R latch	$Q^* = S + R' \cdot Q$
D latch	$Q^* = D$
Edge-triggered D flip-flop	$Q^* = D$
D flip-flop with enable	$Q^* = EN \cdot D + EN' \cdot Q$
Edge-triggered J-K flip-flop	$Q^* = J \cdot Q' + K' \cdot Q$
T flip-flop	$Q^* = Q'$
T flip-flop with enable	$Q^* = EN \cdot Q' + EN' \cdot Q$

Analysis of State Machines with D Flip-Flops

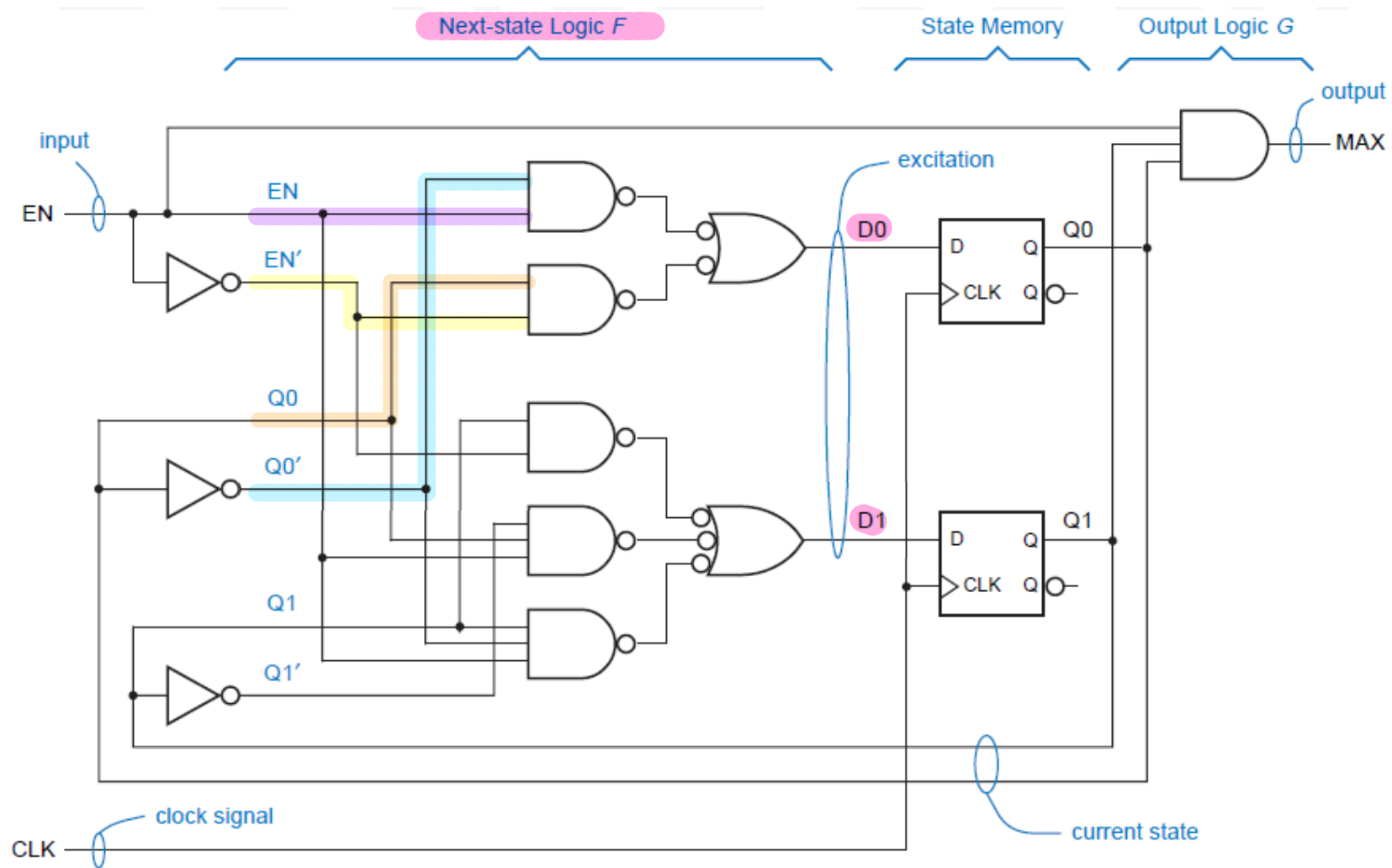
1. Determine the next state and output functions F and G .
2. Use F and G to construct a state / output table that completely specifies the next state and Output of the circuit for every possible combination of current state and input.
3. (Optional) Draw a State diagram that presents the information from the previous step in graphical form.



$$D0 = Q0 \cdot EN' + Q0' \cdot EN$$

$$D1 = Q1 \cdot EN' + Q1' \cdot Q0 \cdot EN + Q1 \cdot Q0' \cdot QN$$

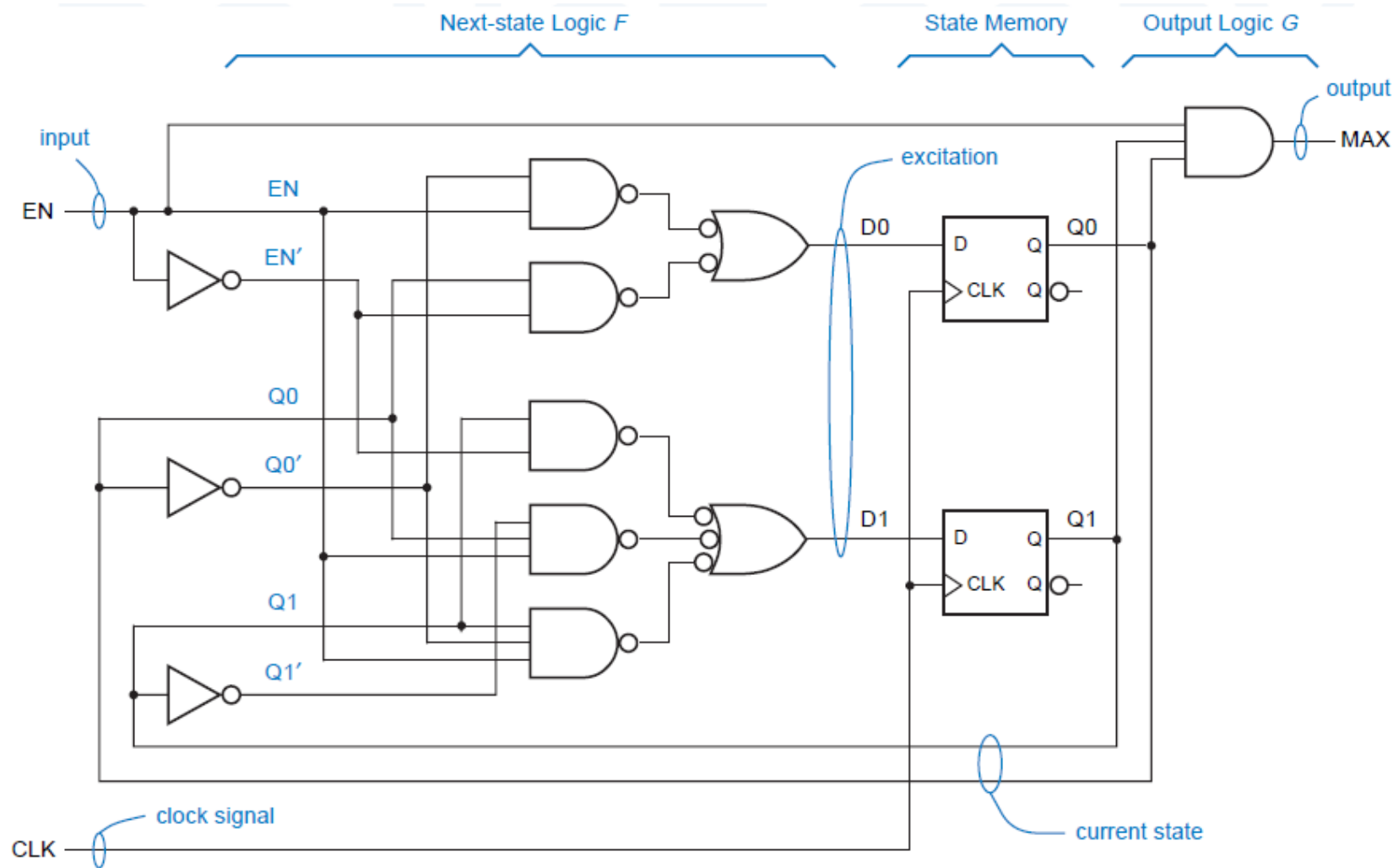Clocked synchronous state machine using positive-edge-triggered D flip-flops



The next value of a state variable after a clock tick is denoted by appending a star to the state-variable name.


$$Q0^* = D0$$

$$Q1^* = D1$$

$$Q0^* = Q0 \cdot EN' + Q0' \cdot EN$$

$$Q1^* = Q1 \cdot EN' + Q1' \cdot Q0 \cdot EN + Q1 \cdot Q0' \cdot QN$$

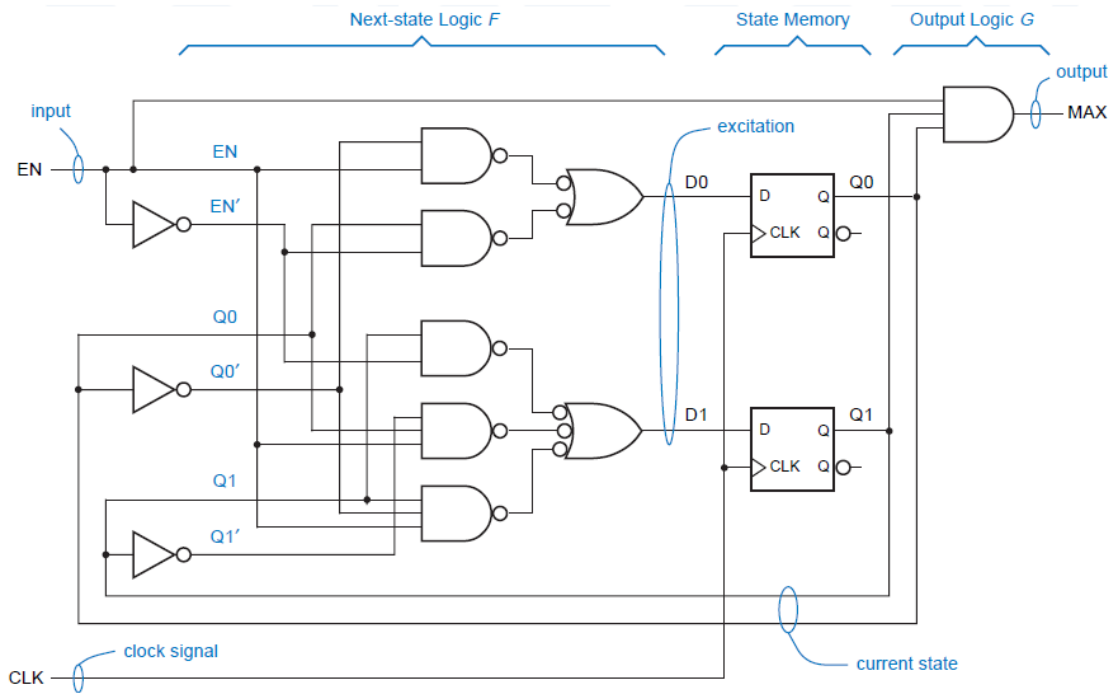Clocked synchronous state machine using positive-edge-triggered D flip-flops



Clocked synchronous state machine using positive-edge-triggered D flip-flops

Q1 Q0	EN	
	0	1
0 0	00	01
0 1	01	10
1 0	10	11
1 1	11	00
Q1* Q0*		

Transition table




S	EN	
	0	1
A	A	B
B	B	C
C	C	D
D	D	A
S*		

State table

K-map

S	EN	
	0	1
A	A,0	B,0
B	B,0	C,0
C	C,0	D,0
D	D,0	A,1
S* , MAX		

State/output table


 


$$MAX = Q1 \cdot Q0 \cdot EN$$

S	EN	
	0	1
A	A, 0	B, 0
B	B, 0	C, 0
C	C, 0	D, 0
D	D, 0	A, 1

S^*, MAX


State/output table

  


State diagram

- A state diagram presents the information from the state / output table in a graphical format.
- A circle (or **node**) for each state.
- An arrow (or **directed arc**) for each transition.

Redrawn

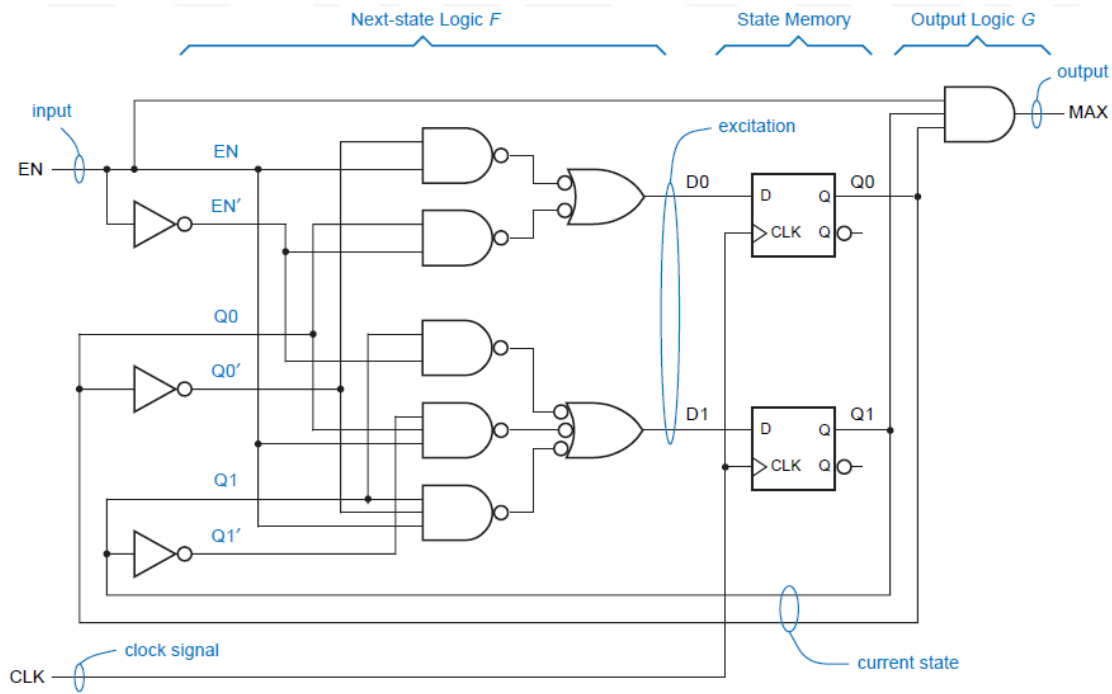

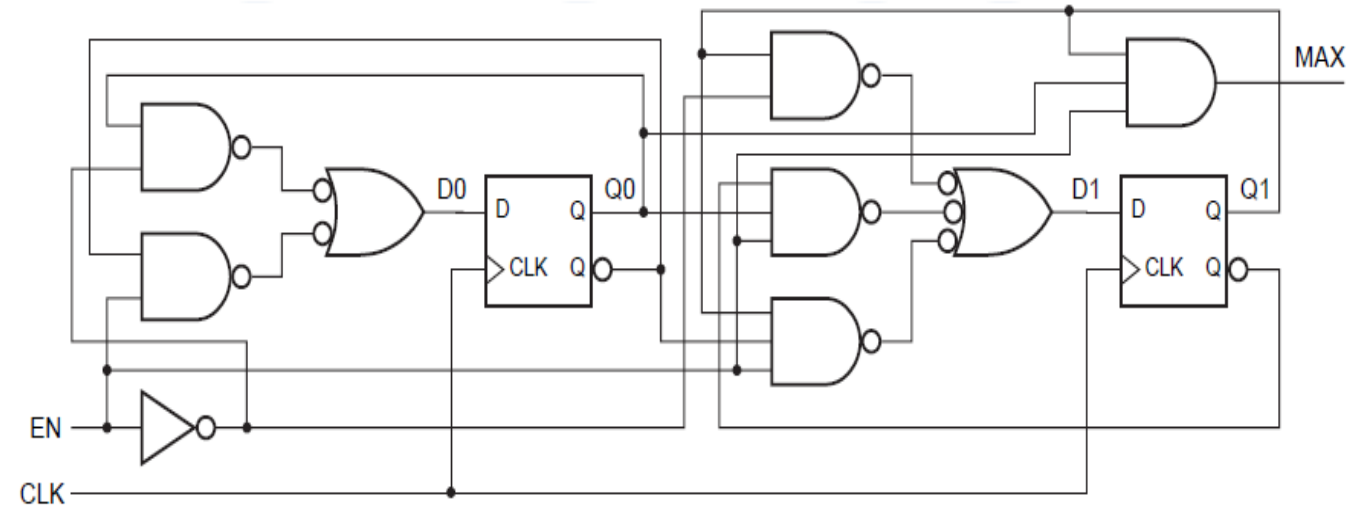Clocked synchronous state machine
using positive-edge-triggered D flip-flops




Redrawn logic diagram for a clocked
synchronous state machine



S	EN	
	0	1
A	A, 0	B, 0
B	B, 0	C, 0
C	C, 0	D, 0
D	D, 0	A, 1
S*, MAX		

$$MAX = Q1 \cdot Q0 \cdot EN$$

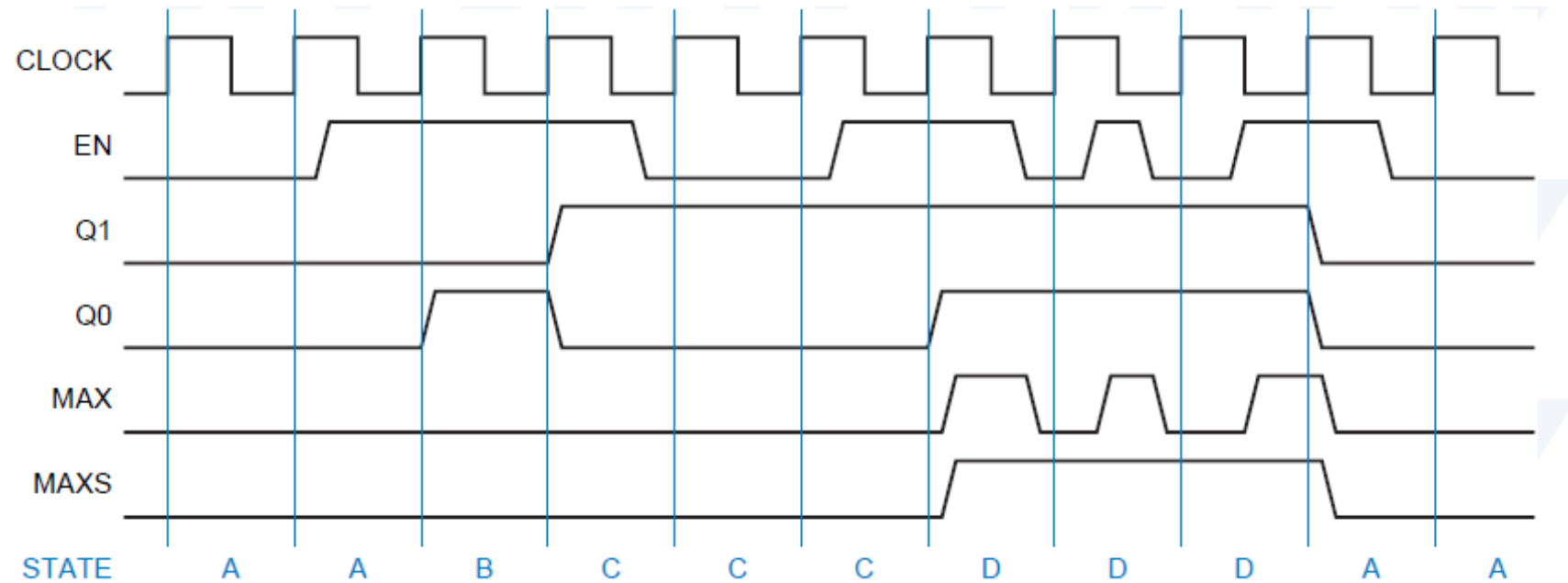


Timing diagram for example state machine

Summarizing detailed steps for analyzing a clocked synchronous state machine


(ทำให้เห็นสถานะได้)

1. Determine the excitation equations for the flip-flop control inputs.
2. Substitute (แทนที่) the excitation equations into the flip-flop characteristic equations to obtain transition equations.
3. Use the transition equations to construct a transition table.
4. Determine the output equations.
5. Add output value to the transition table for each state (Moore) or state / input combination (Mealy) to create a transition/output table.
6. Name the states and substitute state names for state-variable combinations in the transition/output table to obtain a state/output table.
7. (Optional) Draw a state diagram corresponding to the state/output table.

Another example

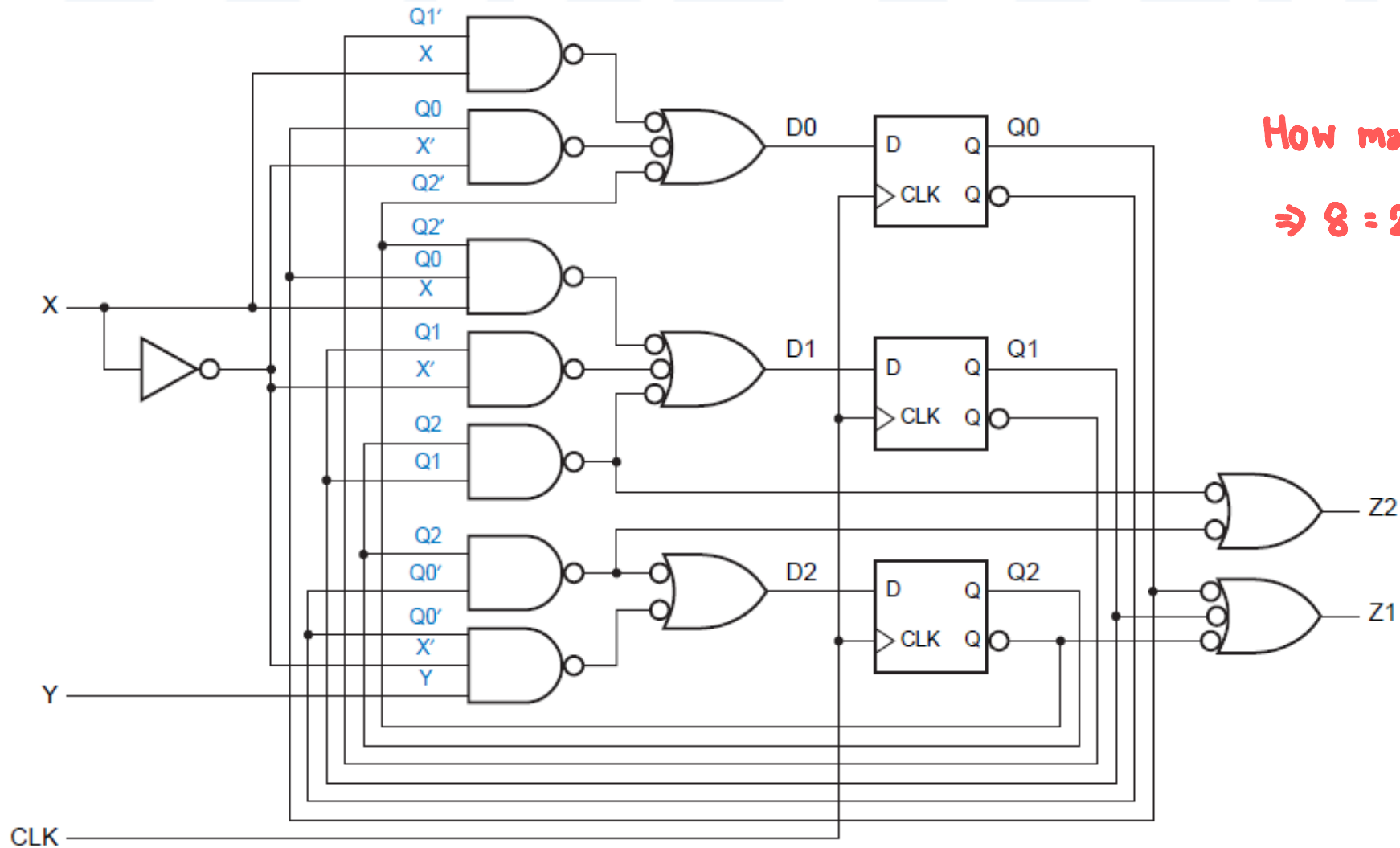

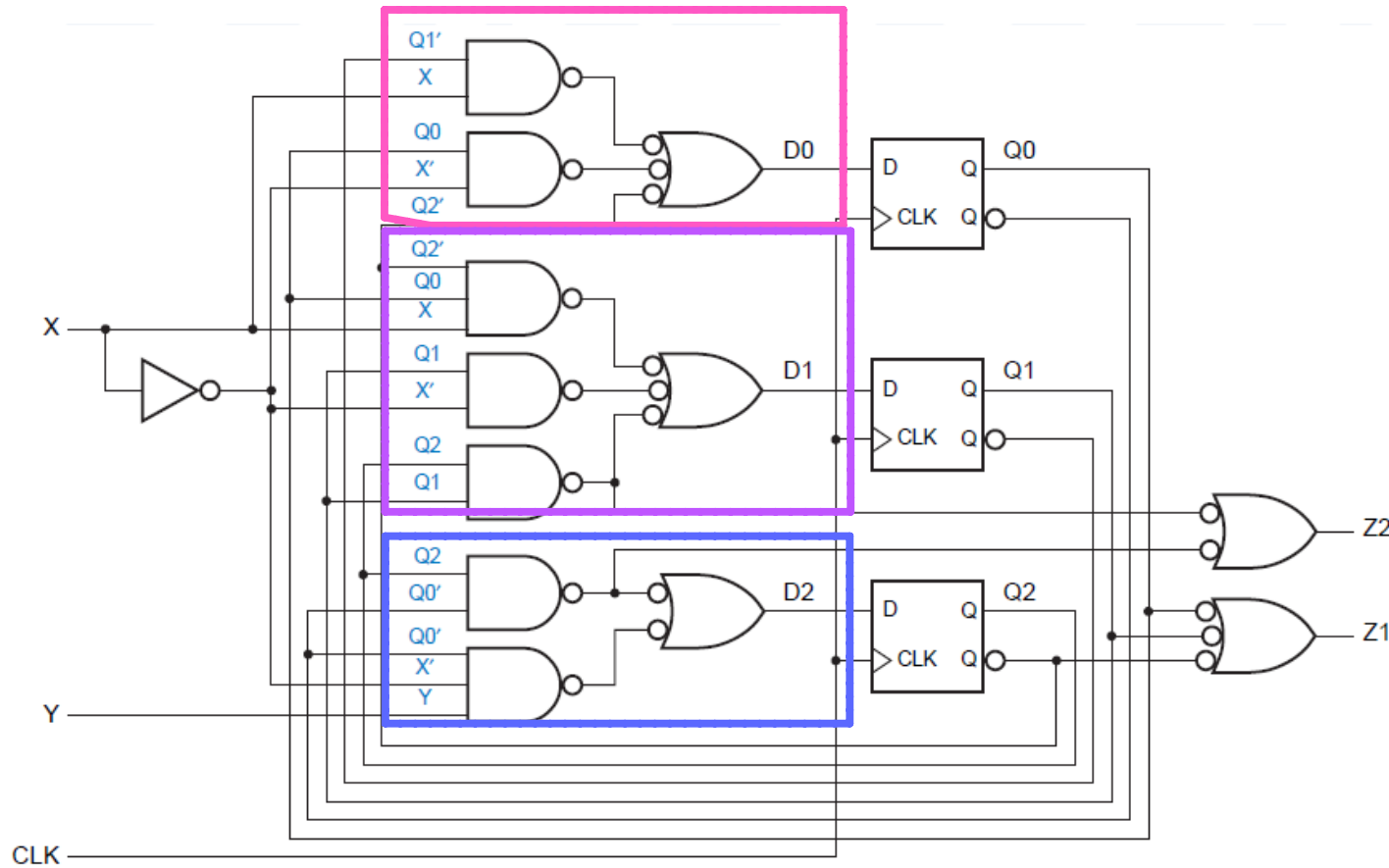How many state this logic diagram
 $\Rightarrow 8 = 2^3$



The excitation equations are :

$$D0 = Q1' \cdot X + Q0 \cdot X' + Q2$$

$$D1 = Q2 \cdot Q0 \cdot X + Q1 \cdot X' + Q2 \cdot Q1$$

$$D2 = Q2 \cdot Q0' + Q0' \cdot X' \cdot Y$$

Substituting into the
characteristic equation
for D flip-flops

$$Q0^* = Q1' \cdot X + Q0 \cdot X' + Q2$$

$$Q1^* = Q2' \cdot Q0 \cdot X + Q1 \cdot X' + Q2 \cdot Q1$$

$$Q2^* = Q2 \cdot Q0' + Q0' \cdot X' \cdot Y$$

$$\begin{aligned} Q0^* &= Q1' \cdot X + Q0 \cdot X' + Q2 \\ Q1^* &= Q2' \cdot Q0 \cdot X + Q1 \cdot X' + Q2 \cdot Q1 \\ Q2^* &= Q2 \cdot Q0' + Q0' \cdot X' \cdot Y \end{aligned}$$

Transition equation



X Y					
Q2 Q1 Q0	00	01	10	11	Z1 Z2
000	000	100	001	001	10
001	001	001	011	011	10
010	010	110	000	000	10
011	011	011	010	010	00
100	101	101	101	101	11
101	001	001	001	001	10
110	111	111	111	111	11
111	011	011	011	011	11
Q2* Q1* Q0*					

Transition/output table

$$\begin{aligned} Z1 &= Q2 + Q1' + Q0' \\ Z2 &= Q2 \cdot Q1 + Q2 \cdot Q0' \end{aligned}$$

Two output equation



X Y					
S	00	01	10	11	Z1 Z2
A	A	E	B	B	10
B	B	B	D	D	10
C	C	G	A	A	10
D	D	D	C	C	00
E	F	F	F	F	11
F	B	B	B	B	10
G	H	H	H	H	11
H	D	D	D	D	11
S*					

State/output table


$$Z1 = Q2 + Q1' + Q0'$$

$$Z2 = Q2 \cdot Q1 + Q2 \cdot Q0'$$

Two output equation

S	XY				Z1 Z2
	00	01	10	11	
A	A	E	B	B	10
B	B	B	D	D	10
C	C	G	A	A	10
D	D	D	C	C	00
E	F	F	F	F	11
F	B	B	B	B	10
G	H	H	H	H	11
H	D	D	D	D	11

State/output table

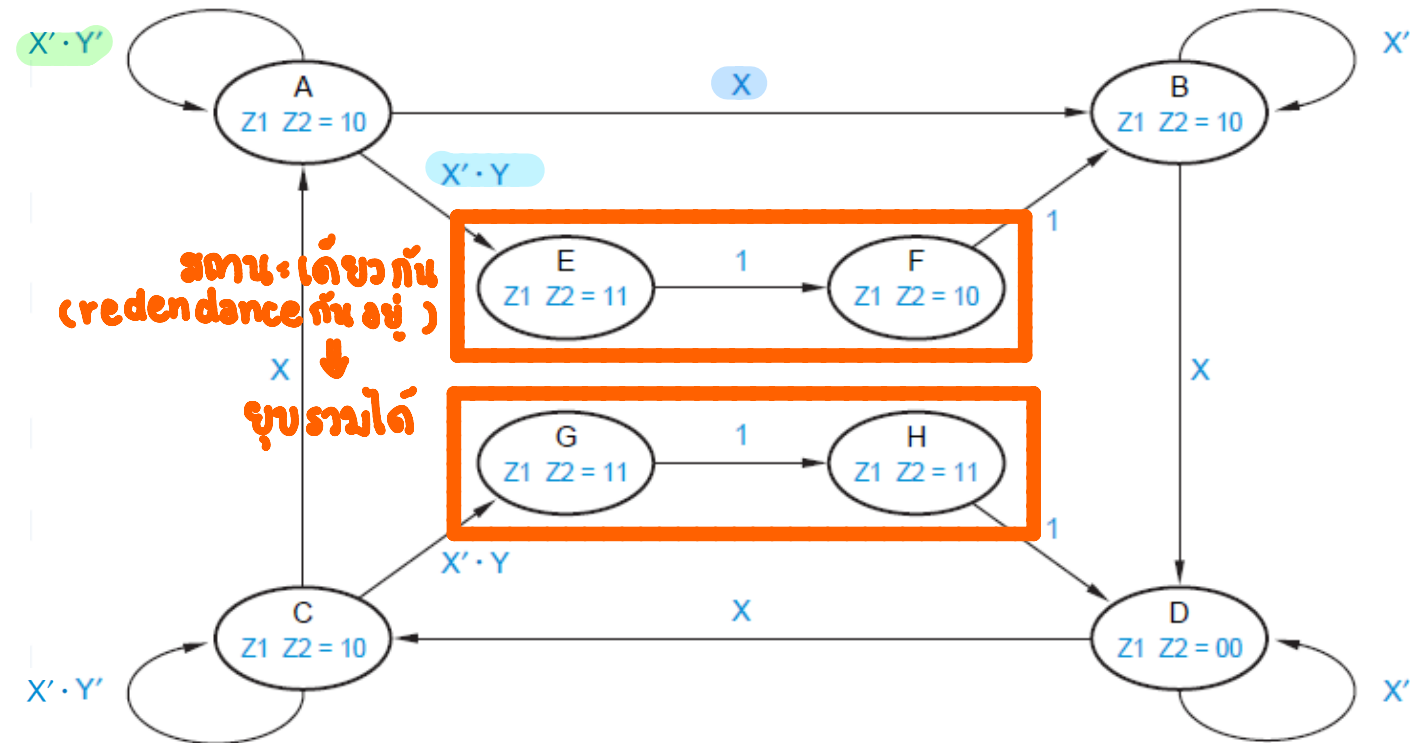

State diagram

Transition expression constraints

- No Two transition can equal 1 for the same input combination since a machine cannot have two next state for one input combination.
- For every possible input combination, some transition expression must equal 1, so that all next states are defined.

Mutual exclusion

All inclusion

“The transition expressions on arcs leaving a particular state must be mutually exclusive and all inclusive.”