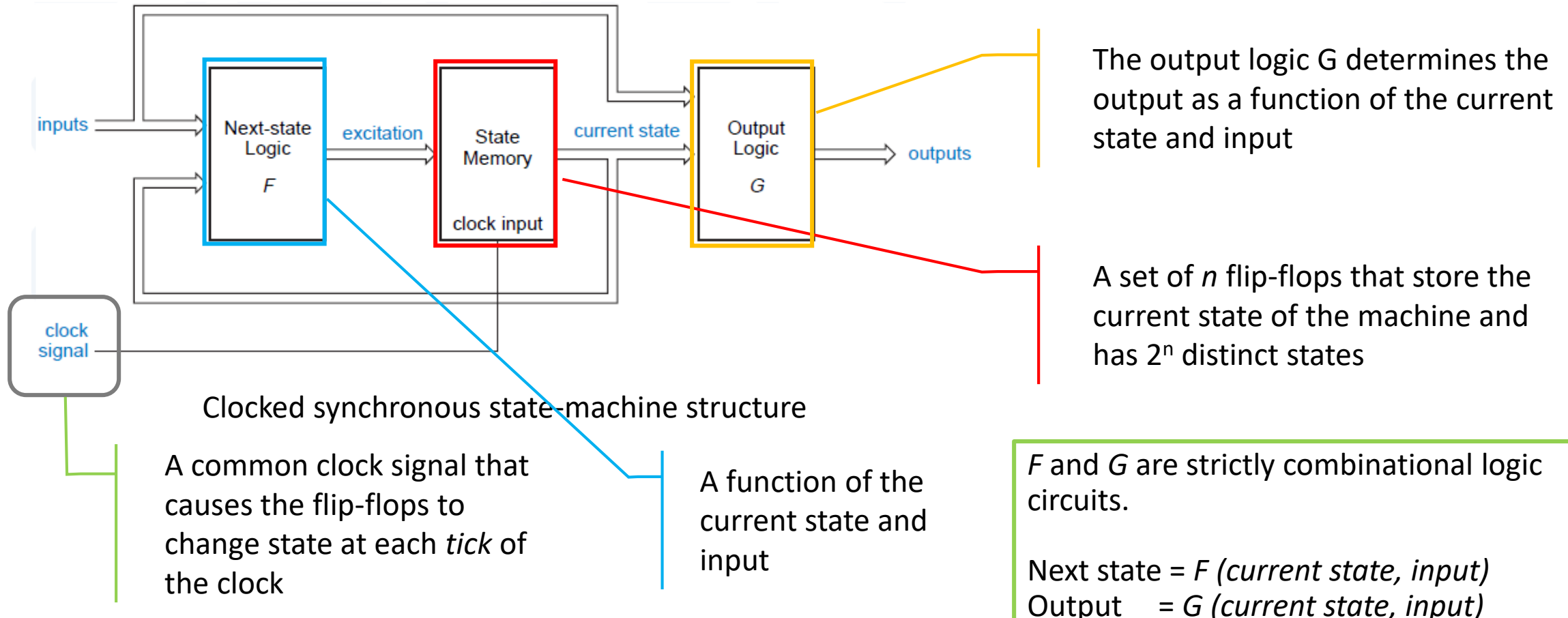


Pakorn Watanachaturaporn
pakorn.wa@KMITL.ac.th


01076244 Advanced Digital System Design

Bachelor Program in Computer Engineering (B.Eng.)
Faculty of Engineering
King Mongkut's Institute of Technology Ladkrabang


State-Machine Structure



Output Logic

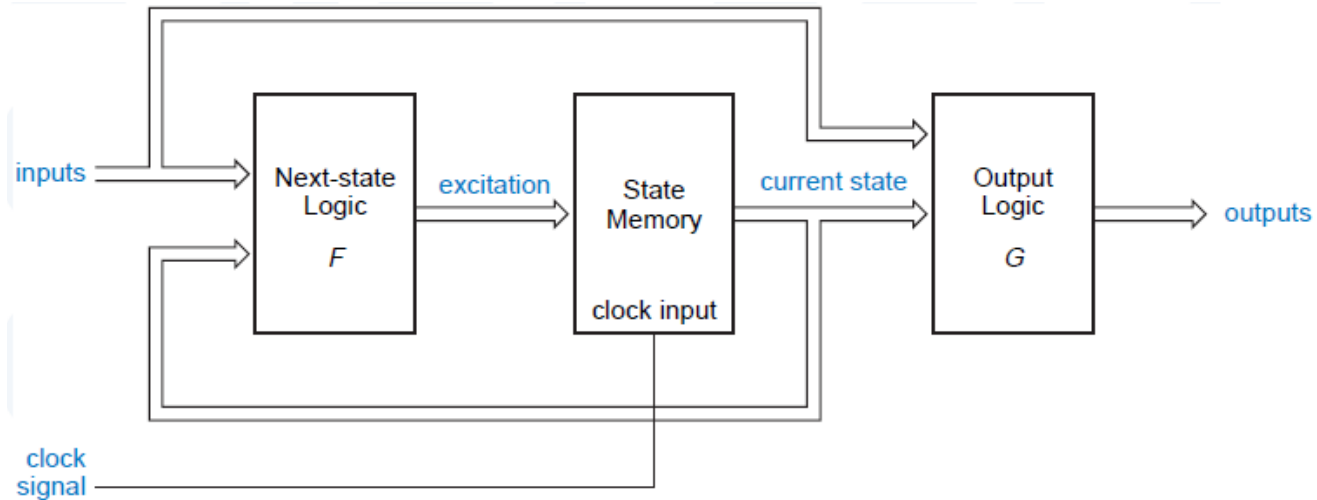

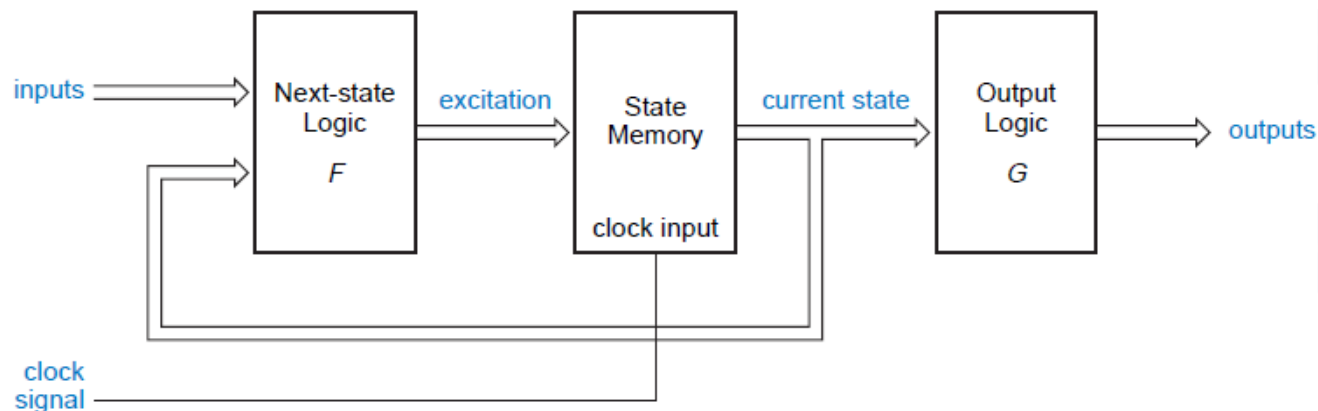Mealy machine : output depends on both state and input



Moore machine : the output depends on state alone


Characteristic Equations

- A _____ is a formally description of a _____
- The _____ suffix means the “_____”
- Note: the characteristic equation does not describe detailed timing behavior of the device (latching vs. edge-triggered, etc.), only _____

Device Type	Characteristic Equation
S-R latch	$Q^* = S + R' \cdot Q$
D latch	$Q^* = D$
Edge-triggered D flip-flop	$Q^* = D$
D flip-flop with enable	$Q^* = EN \cdot D + EN' \cdot Q$
Edge-triggered J-K flip-flop	$Q^* = J \cdot Q' + K' \cdot Q$
T flip-flop	$Q^* = Q'$
T flip-flop with enable	$Q^* = EN \cdot Q' + EN' \cdot Q$

Analysis of State Machines with D Flip-Flops

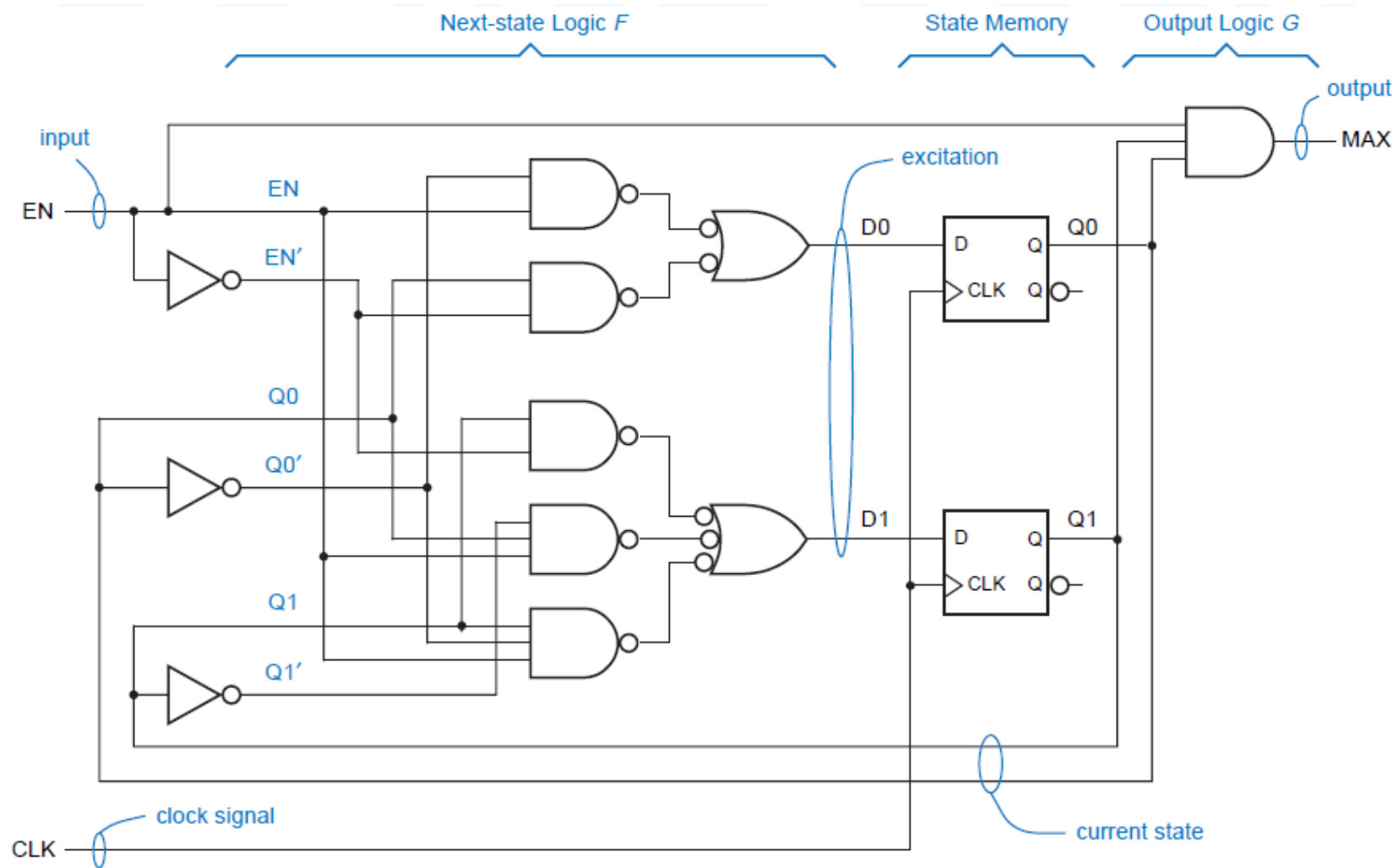
1. Determine the _____ and _____ F and G .
2. Use F and G to construct a _____ that completely specifies the _____ and _____ of the circuit for every possible combination of current state and input.
3. (Optional) Draw a _____ that presents the information from the previous step in graphical form.



$D0 =$

$D1 =$

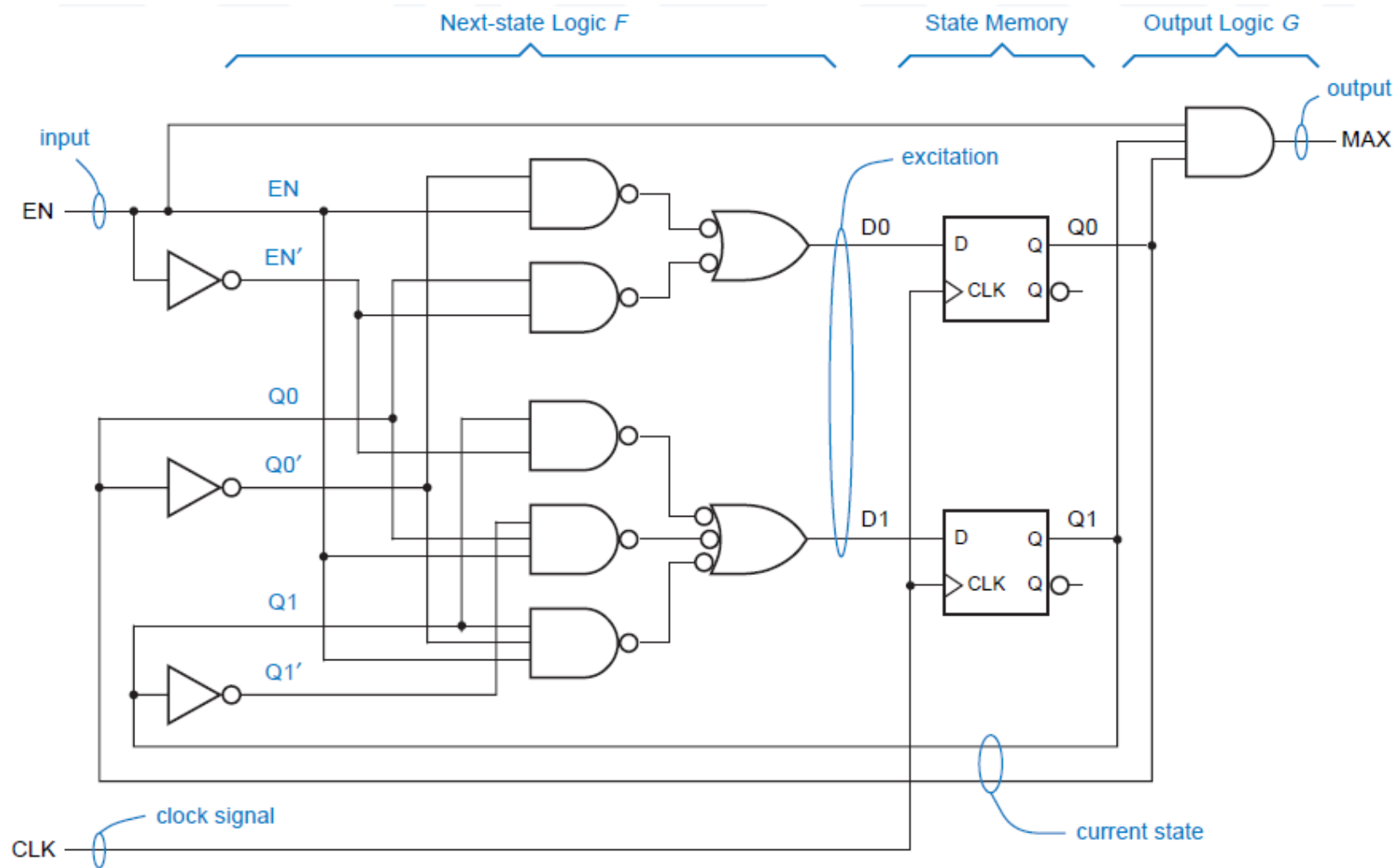Clocked synchronous state machine using positive-edge-triggered D flip-flops



Clocked synchronous state machine using positive-edge-triggered D flip-flops


The _____ after a clock tick is denoted by _____ to the state-variable name.

$Q0^* =$

$Q1^* =$

$Q0^* =$

$Q1^* =$

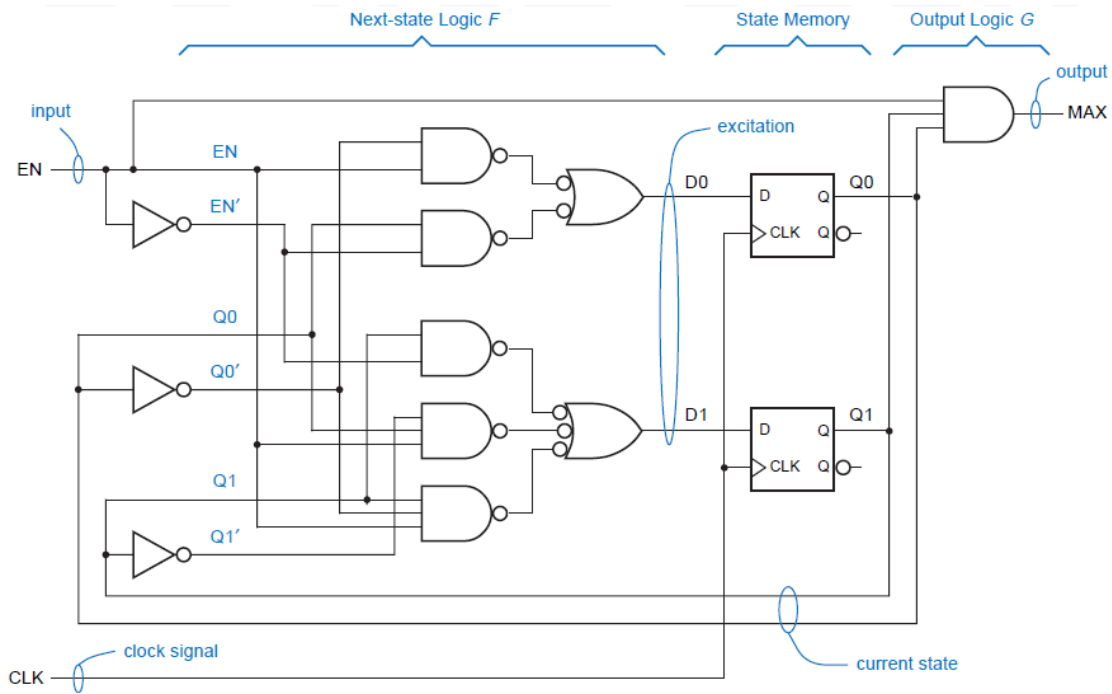

Clocked synchronous state machine using positive-edge-triggered D flip-flops

Q1 Q0		EN	
		0	1
0 0			
0 1			
1 0			
1 1			
		Q1* Q0*	

Transition table




S	EN	
	0	1
A		
B		
C		
D		
	S*	

State table

S	EN	
	0	1
A		
B		
C		
D		
	S*, MAX	



State/output table

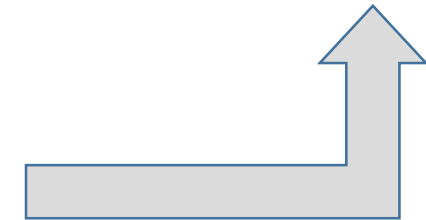

S	EN	
	0	1
A	A, 0	B, 0
B	B, 0	C, 0
C	C, 0	D, 0
D	D, 0	A, 1

S^*, MAX


State/output table

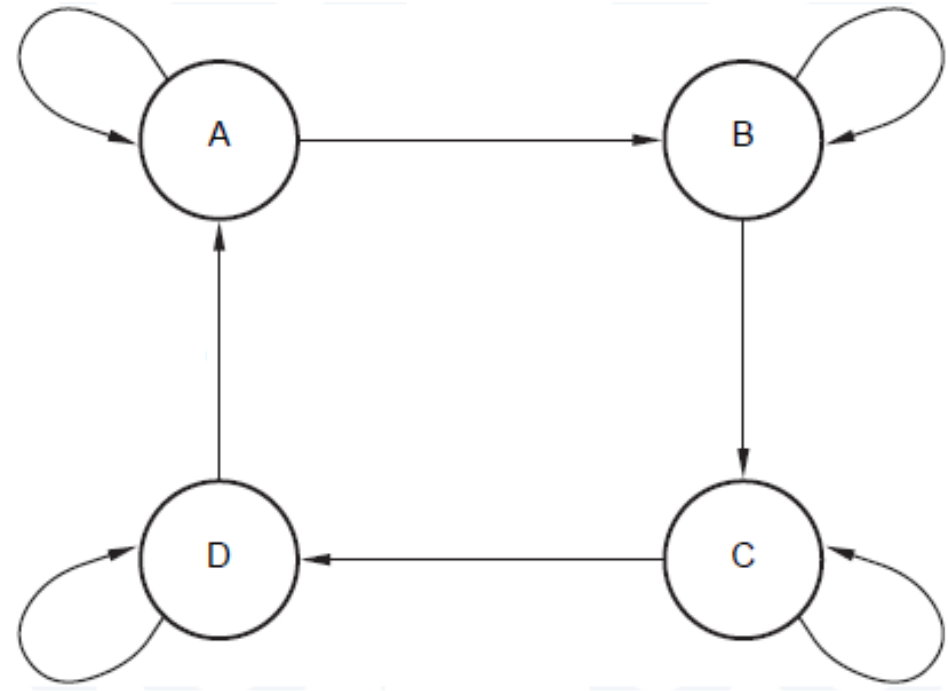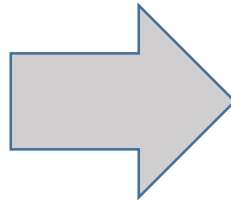


State diagram

- A state presents the information from the table in a graphical format.
- A circle (or oval) for each state.
- An arrow (or directed edge) for each transition.

Redrawn

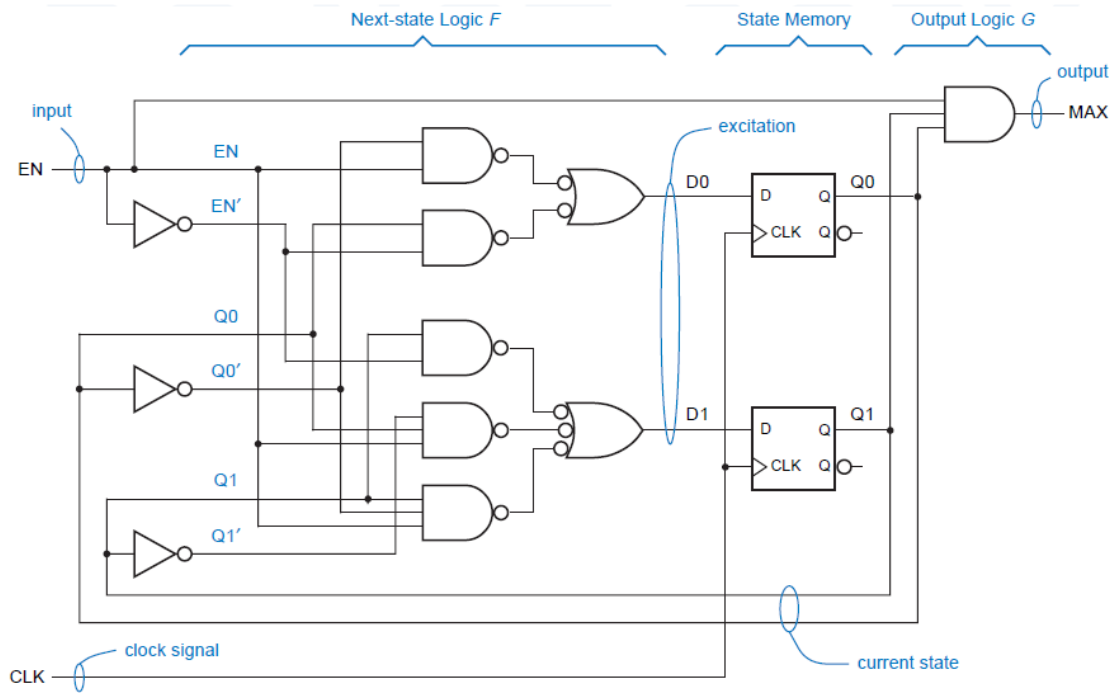

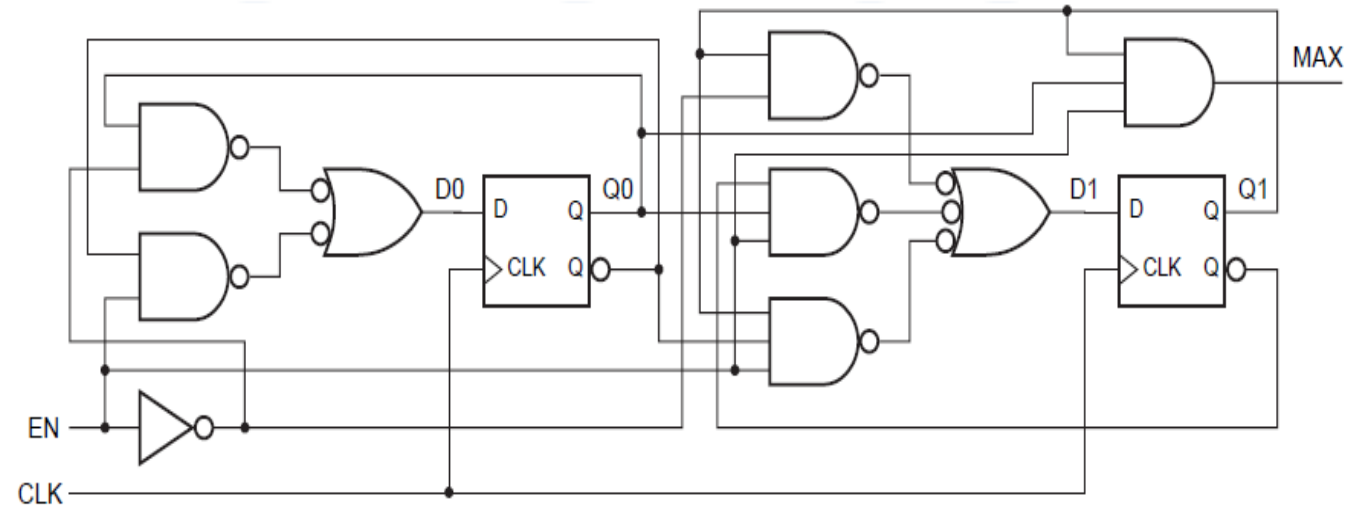Clocked synchronous state machine
using positive-edge-triggered D flip-flops




Redrawn logic diagram for a clocked
synchronous state machine



S	EN	
	0	1
A	A, 0	B, 0
B	B, 0	C, 0
C	C, 0	D, 0
D	D, 0	A, 1
S*, MAX		

$$MAX = Q1 \cdot Q0 \cdot EN$$

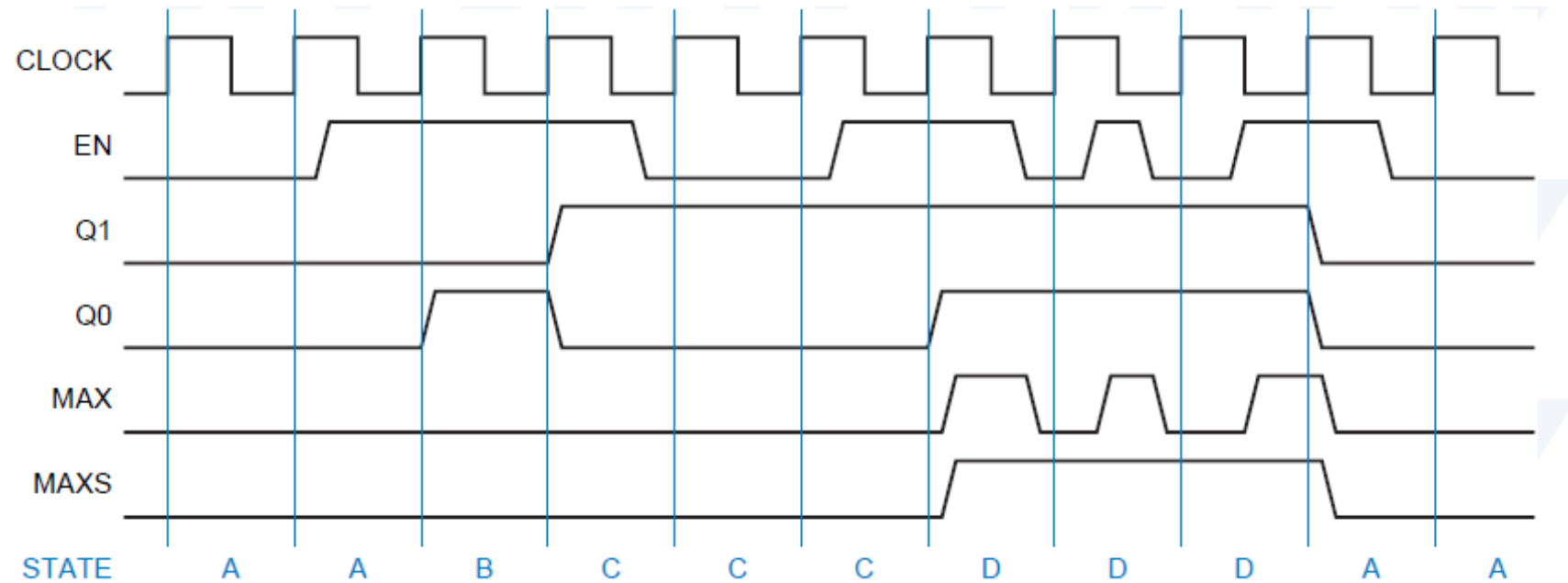



Timing diagram for example state machine

Summarizing detailed steps for analyzing a clocked synchronous state machine

1. Determine _____ for the flip-flop control inputs.
2. _____ the excitation equations into the flip-flop characteristic equations to obtain transition equations.
3. Use the _____ to construct a transition table.
4. Determine the _____.
5. Add _____ to the transition table for each state (Moore) or _____ (Mealy) to create a transition/output table.
6. _____ and _____ for state-variable combinations in the transition/output table to obtain a state/output table.
7. (Optional) Draw a state diagram corresponding to the state/output table.

Another example

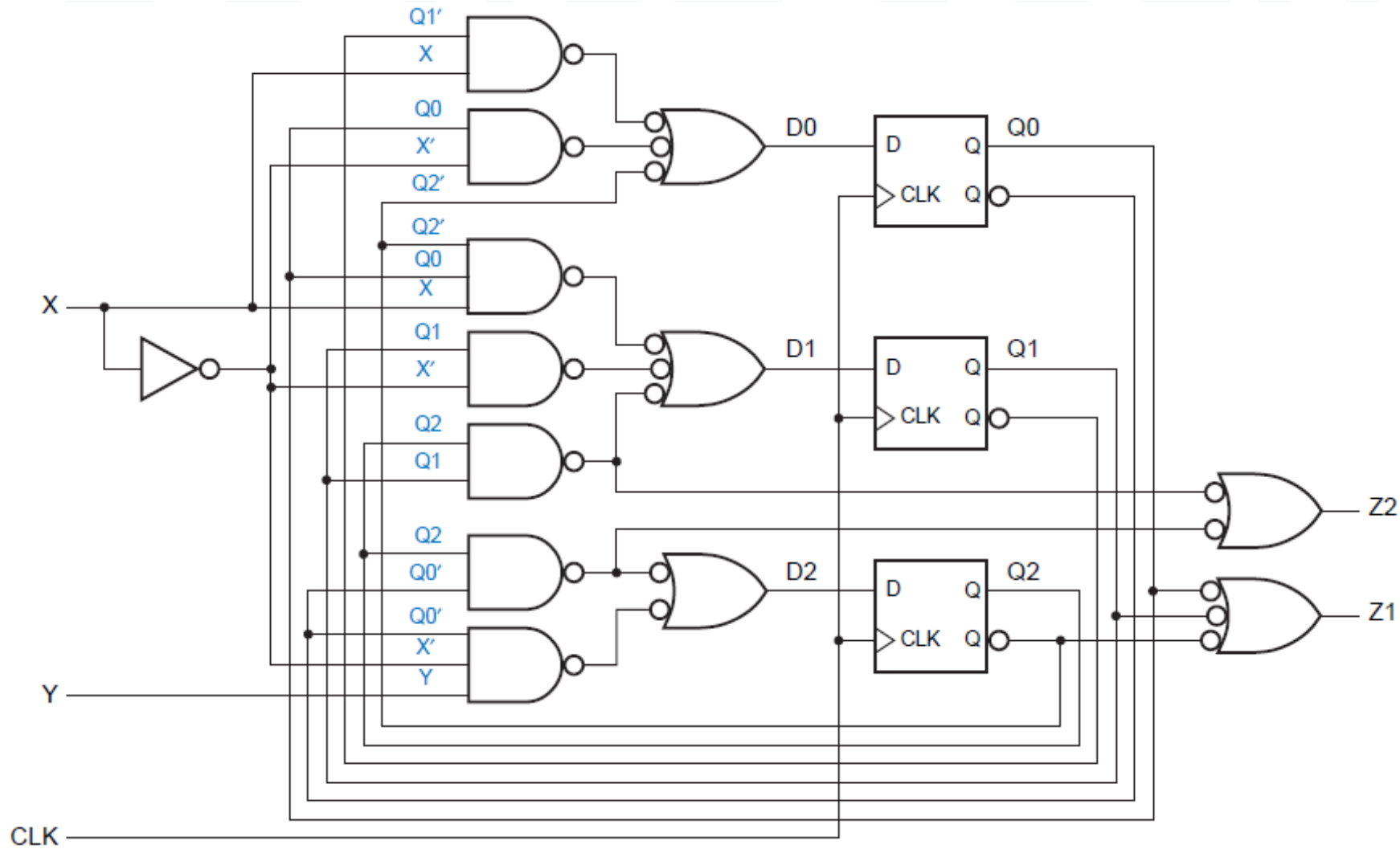

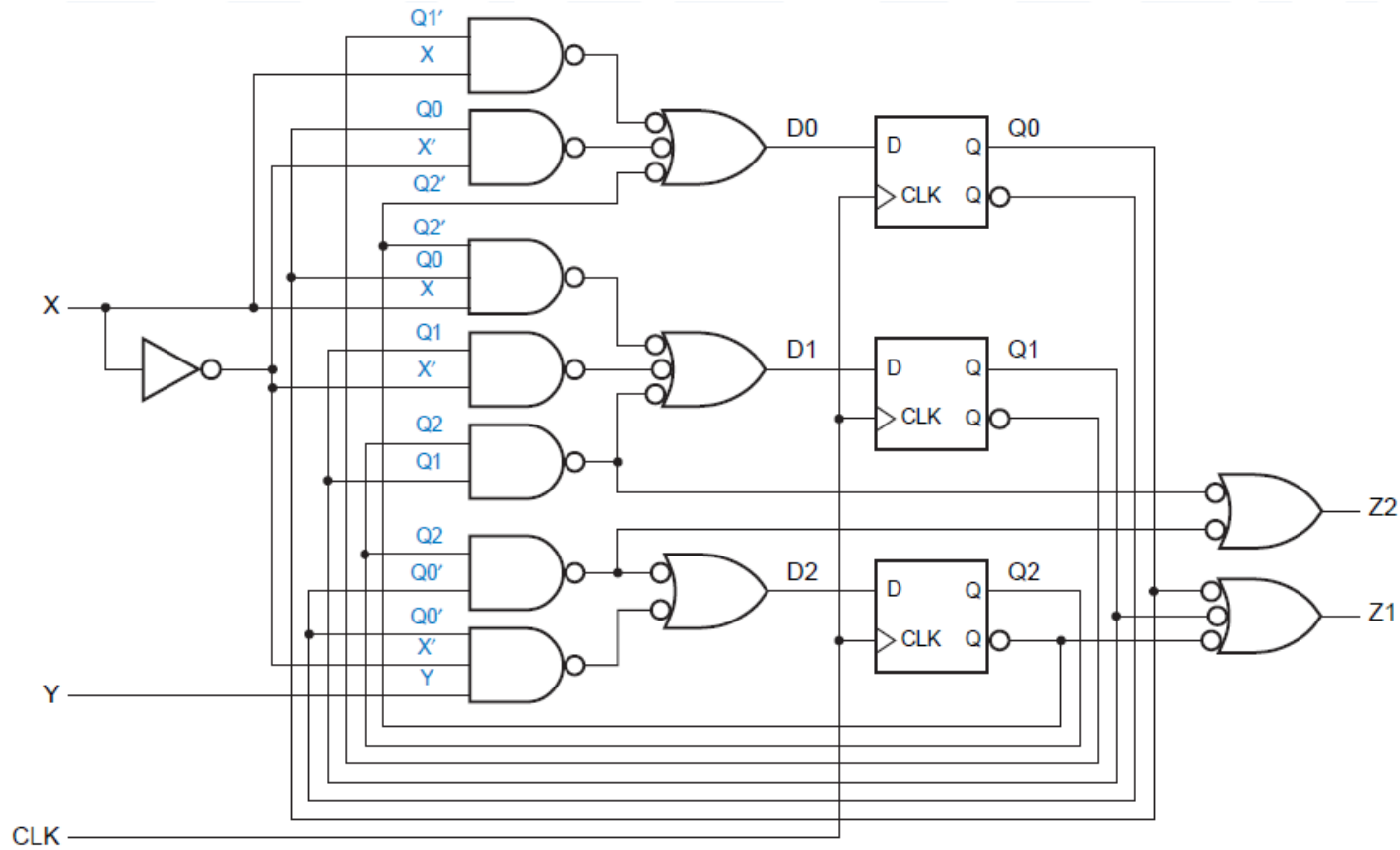

The excitation equations are :

$$\begin{aligned} Q0^* &= Q1' \cdot X + Q0 \cdot X' + Q2 \\ Q1^* &= Q2' \cdot Q0 \cdot X + Q1 \cdot X' + Q2 \cdot Q1 \\ Q2^* &= Q2 \cdot Q0' + Q0' \cdot X' \cdot Y \end{aligned}$$

Transition equation



Q2 Q1 Q0	X Y				Z1 Z2
	00	01	10	11	
000	000	100	001	001	10
001	001	001	011	011	10
010	010	110	000	000	10
011	011	011	010	010	00
100	101	101	101	101	11
101	001	001	001	001	10
110	111	111	111	111	11
111	011	011	011	011	11
Q2* Q1* Q0*					

Transition/output table

$$\begin{aligned} Z1 &= Q2 + Q1' + Q0' \\ Z2 &= Q2 \cdot Q1 + Q2 \cdot Q0' \end{aligned}$$

Two output equation



S	X Y				Z1 Z2
	00	01	10	11	
A	A	E	B	B	10
B	B	B	D	D	10
C	C	G	A	A	10
D	D	D	C	C	00
E	F	F	F	F	11
F	B	B	B	B	10
G	H	H	H	H	11
H	D	D	D	D	11
S*					

State/output table

$$Z1 = Q2 + Q1' + Q0'$$


$$Z2 = Q2 \cdot Q1 + Q2 \cdot Q0'$$

Two output equation

S	XY				Z1 Z2
	00	01	10	11	
A	A	E	B	B	10
B	B	B	D	D	10
C	C	G	A	A	10
D	D	D	C	C	00
E	F	F	F	F	11
F	B	B	B	B	10
G	H	H	H	H	11
H	D	D	D	D	11

S*

State/output table

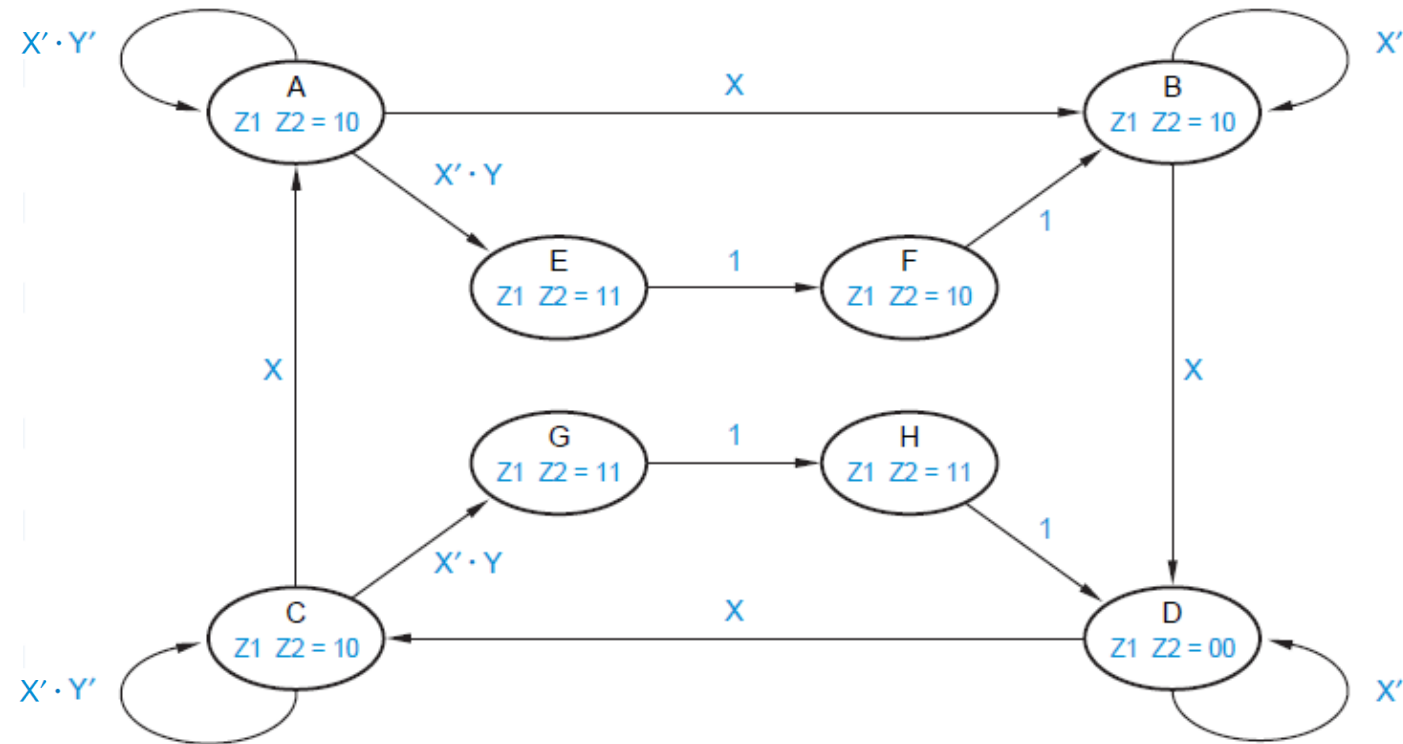

State diagram

Transition expression constraints

- _____ can equal 1 for the same input combination since a machine cannot have _____ for one input combination.
- For every possible _____, some _____ must equal 1, so that all next states are defined.

“The transition expressions on arcs leaving a particular state must be _____ and _____.”